



Figure 3 This circuit enhances the one in Figure 2 by adding an inexpensive 4053 analog switch, allowing bidirectional switching.