



Figure 1 A transformer and a relay are all you need to control a secondary load should the main load fail.