



Figure 1 You can switch the on-die termination and select the effective value through a pullup/pulldown-resistor network.

---