



Figure 1 This DAC-controlled 4- to 20-mA transmitter allows digital control of the loop current.