



Figure 1 A typical voltage regulator lets you set the regulated output level by adjusting the  $R_1/R_2$  divider.