



Figure 2 Connecting one-half of a dual variable resistor in parallel with R_2 to the circuit in Figure 1 lets you temperature-compensate the regulated output voltage.