



**Figure 1** This dark-activated switch needs only a photocell, a resistor, and a triac to switch between the ac line and the device.