



Figure 1 Driven by a 0 to 2.048V music signal at pins 12 and 1 of IC₁, this circuit activates the six ac outlets according to the music amplitude, in a logarithmic thermometer-code format (a). The power block (b) represents each of the power blocks, PB₁ through PB₆.