



Figure 1 You can build a simple pulse generator with just two commonly available ICs.