



Figure 1 A 555 timer provides the necessary pulses for configuring an LED driver.