



Figure 1 A typical adder configuration uses a single op amp.