



Figure 2 Two instrumentation amplifiers provide increased input impedance in this adder circuit.