



**Figure 1** Lumped-element models typically represent transmission lines, with successive infinitesimal segments, interconnected by an ideal transmission line, having series resistance  $R$ , series inductance  $L$ , shunt conductance  $G$ , and shunt capacitance  $C$ , from which you can calculate characteristic impedance. Your switch should offer the same characteristic impedance.

---