



Figure 1 The resistive DAC-potentiometer forming the feedback for an op amp controls the op amp's gain as inversely proportional to the digital-input-data word. The circuit thus becomes a two-quadrant divider.