



Figure 4 This circuit doesn't work because the comparator has insufficient head room. The inputs are too close to the positive rail.

---