



Figure 5 A rail-to-rail input part has two input stages. With bipolar parts, the input-bias current reverses direction as the input common-mode voltage sweeps through the input range (courtesy Analog Devices).