



**Figure 6** You should terminate fast comparator outputs to prevent ringing and reflections. You can use shunt (a), series (b), ac (c), or differential (d) termination.