



Figure 1 Use delta-sigma converters to implement process gain and level-shifting on an analog signal.