



**Figure 2** On a positive half-cycle, current flows from  $Q_3$  through  $C_1$  to a load (a). On a negative half-cycle, current flows through  $Q_4$ .