



Figure 3 A typical application of this Class B circuit is a headphone amplifier.