



**Figure 1** Using two MOSFETs to differentially drive a dual-coil latching relay eliminates the need for any logic components.