



**Figure 2**

**NOTE:**  
ALL NORMALIZED INDUCTORS AND CAPACITORS EQUAL 1.

**By judicious connection of components, this filter uses only one value each for the inductors and capacitors.**