Figure 1

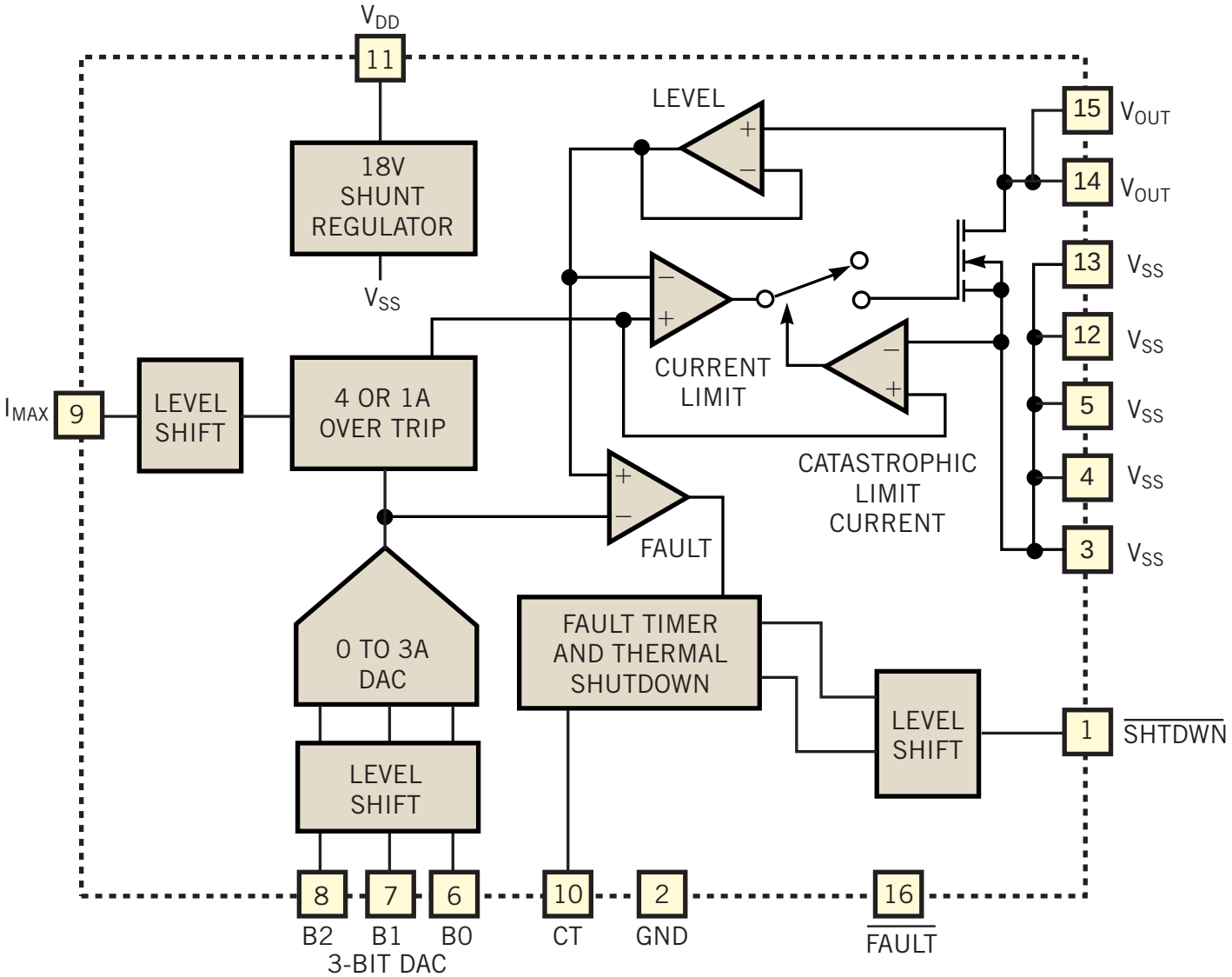

A 3-bit DAC in Unitrode's UCC3920 hot-swap manager allows you to program the fault-level trip current that suits your system.