Figure 1

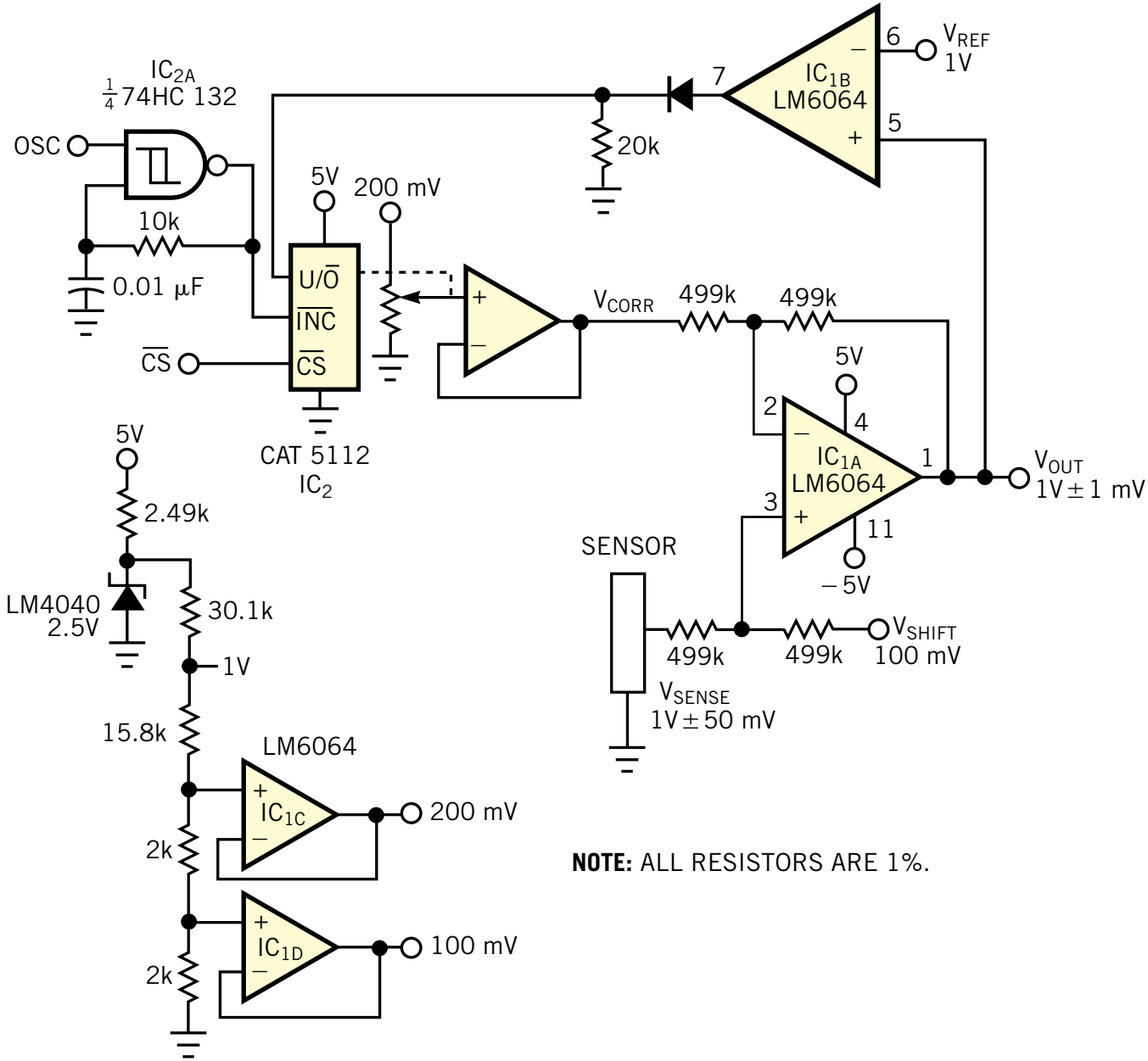

The autoreferencing circuit nulls out output errors at a sensor's reference (ambient) condition.